

Practical Phase-Locked Loop Design

2004 ISSCC Tutorial

Dennis Fischette

Email: pll@delroy.com

Website: <http://www.delroy.com/pll>

Outline

- Introduction
- Basic Feedback Loop Theory
- Circuits
- “Spectacular” Failures
- Appendices:
 - design for test
 - writing a PLL Spec
 - references
- Sorry: no DLL’s in this tutorial

Intended Audience

- If you...
- Are a novice PLL designer
- Specify PLL requirements
- Integrate PLL's on-chip
- Test/debug PLL's
- Review PLL designs

Introduction


What is a PLL?

- A PLL is a negative feedback system where an oscillator-generated signal is phase and frequency locked to a reference signal.
- Analogous to a car's "cruise control"

How are PLL's Used?

- Frequency Synthesis (e.g. generating a 1 GHz clock from a 100 MHz reference)
- Skew Cancellation (e.g. phase-aligning an internal clock to the IO clock) (May use a DLL instead)
- Extracting a clock from a random data stream (e.g. serial-link receiver)
- ***Frequency Synthesis*** is the focus of this tutorial.

Charge-Pump PLL Block Diagram

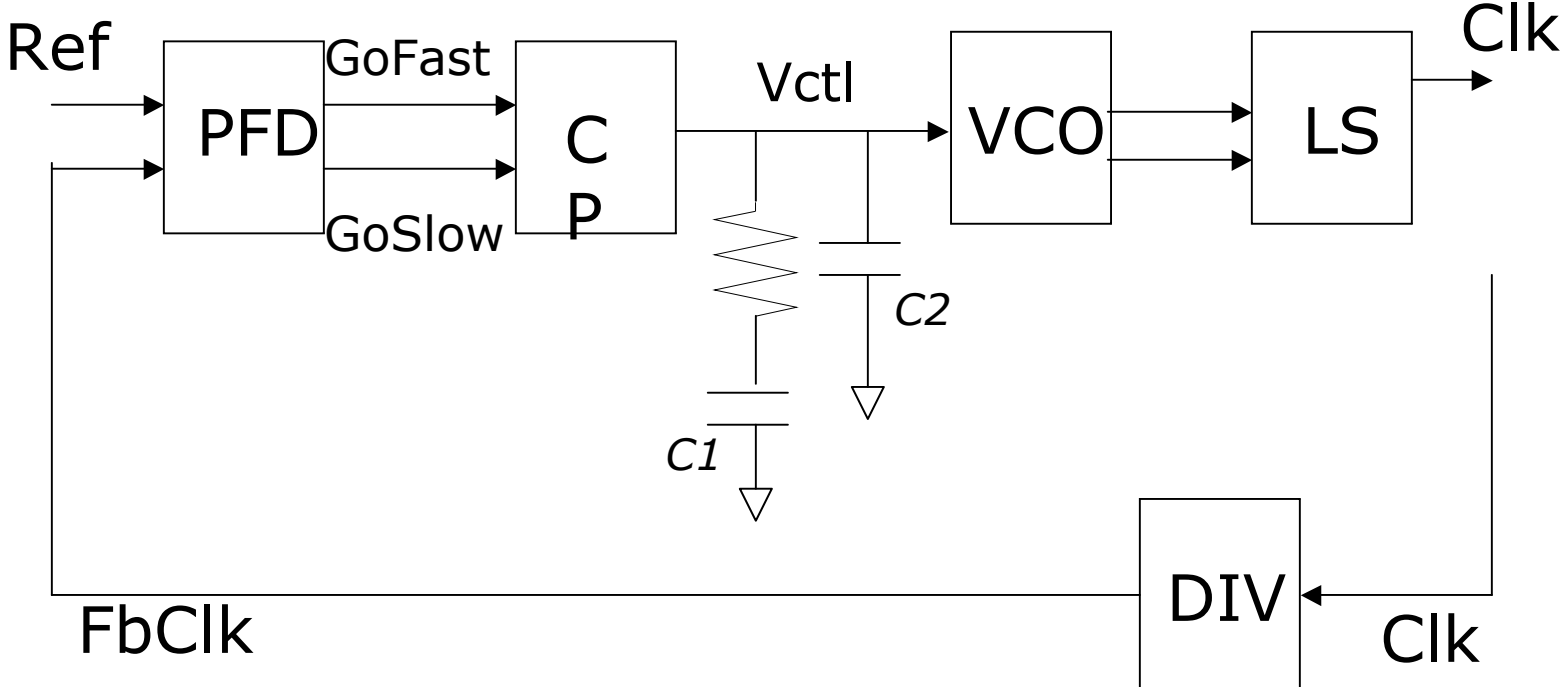

Charge-Pump PLL Building Blocks

- Phase-Frequency Detector (*PFD*)
- Charge-Pump (*CP*)
- Low-Pass Filter (*LPF*)
- Voltage-Controlled Oscillator (*VCO*)
- VCO Level-Shifter (*LS*)
- Feedback Divider (*FBDIV*)
- Power Supply regulator/filter (*VREG*)?

Components in a Nutshell

- PFD: outputs digital pulse whose width is proportional to phase error
- CP: converts digital error pulse to analog error current
- LPF: integrates (and low-pass filters) error current to generate VCO control voltage
- VCO: low-swing oscillator with frequency proportional to control voltage
- LS: amplifies VCO levels to full-swing
- DIV: divides VCO clock to generate FBCLK clock

PLL Feedback Loop Theory

Is My PLL Stable?

- PLL is 2nd-order system similar to mass-spring-dashpot or RLC circuit.
- PLL may be stable or unstable depending on phase margin (or damping factor).
- Phase margin is determined from linear model of PLL in frequency-domain.
- Find phase margin/damping using MATLAB, loop equations, or simulations.
- Stability affects phase error, settling, jitter.

What Does PLL Bandwidth Mean?

- PLL acts as a low-pass filter with respect to the reference.
- Low-frequency reference modulation (e.g. spread-spectrum clocking) is passed to the VCO clock.
- High-frequency reference jitter is rejected.
- “Bandwidth” is the frequency at which the PLL begins to lose lock with the reference (-3dB).
- PLL acts as a high-pass filter wrt VCO noise.
- Bandwidth affects phase error, settling, jitter.

Closed-loop PLL Transfer Function

- Analyze PLL feedback in frequency-domain
- Assumes continuous-time behavior
- $H(s) = \omega_{fb} / \omega_{ref} = G(s) / (1 + G(s)) \rightarrow$ closed-loop gain
- $G(s) = (K_{vco} / s) I_{cp} F(s) / M \rightarrow$ open-loop gain

where

K_{vco} = VCO gain in Hz/V

I_{cp} = charge pump current in Amps

$F(s)$ = loop filter transfer function

M = feedback divisor

C_1 = large loop-filter capacitor

Closed-loop PLL Transfer Function

- General Form (ignoring C_2):

$$H(s) = \omega_n^2 (1 + s/\omega_z) / (s^2 + 2s\zeta\omega_n + \omega_n^2)$$

where

$$\omega_n = \text{natural freq} = \text{sqrt}(K_{\text{vco}}I_{\text{cp}}/MC_1)$$

$$\omega_z = \text{stabilizing zero} = 1 / RC_1$$

$$\zeta = \text{damping} =$$

$$(RC_1/2) * \text{sqrt}(K_{\text{vco}}I_{\text{cp}}/MC_1)$$

- If $\zeta < 1$, complex poles at $-\zeta\omega_n \pm j\omega_n * \text{sqrt}(1 - \zeta^2)$
 - Real \rightarrow exponential delay
 - Imag \rightarrow oscillation

What Determines Stability and Bandwidth?

- Damping Factor (measure of stability)
- Natural Frequency (measure of bandwidth)
- Damping and natural frequency can be set independently by LPF resistor

PLL Loop Equations

- Undamped Natural Frequency:

$$\omega_n = \text{sqrt}(K_{\text{vco}} * I_{\text{cp}} / (M * C_1)) \text{ in rad/sec}$$

where

K_{vco} = VCO gain in Hz/V

I_{cp} = charge pump current in Amps

M = feedback divisor

C_1 = large LPF capacitor

- For stability: $\omega_n / 2\pi < \sim 1/20$ reference frequency
- Typical value: $1 \text{ MHz} < \omega_n / 2\pi < 10 \text{ MHz}$.

PLL Loop Equations

- Damping Factor: usually $0.45 < \zeta < \sim 1.5$

$$\zeta = R_{\text{lpf}} * C_1 * \omega_n / 2$$

- Useful Relation:

$$\text{Phase margin} \sim 100 * \zeta \quad (\text{for } \zeta < 0.65)$$

- Loop Decay Time Constant = $1/(\zeta * \omega_n)$

- used to estimate settling time

- 98% settling in 4 time constants


$$\text{Decay} \sim 1 - \exp(-t * \zeta * \omega_n)$$

PLL Loop Eqns: Limits on R_{lpf}

- PFD must sample faster than loop can respond to act like continuous-time system
- Discrete Time Stability Limit (Gardner, 1980):
$$\omega_n^2 < \omega_{ref}^2 / (\pi * (R_{lpf} C_1 * \omega_{ref} + \pi))$$
- E.g. $\omega_{ref} = 2\pi * 125\text{MHz}$, $C_1 = 75\text{pF}$, $\omega_n = 2\pi * 2\text{MHz}$
 $\rightarrow R_{max} < 21 \text{ kOhm}$
- $R_{lpf} < 1/5 R_{max}$ for good phase margin
- For details: see Gardner (1980), Fig. 4

PLL Loop Eqns: Limits on R_{lpf}

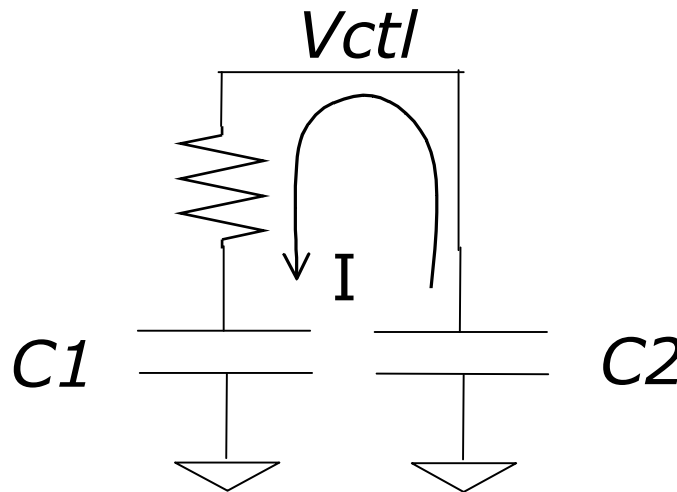- Parasitic LPF Pole: $R_{lpf} * C_2 \sim T_{ref} / \pi$
→ if we want $V(C_1) \sim V(C_2)$ by end of T_{ref} (goal)
(Maneatis ISSCC '03)



$$I = (V_{c2} - V_{c1}) / R$$
$$\tau = RC_2$$

Bode Plot Primer


- Used to analyze frequency domain behavior
- Y-axis: gain in dB. E.g. 20dB=10X gain. 3dB=1.4X
- X-axis: frequency. Log scale
- Assuming “left-hand-plane” location:
 - Pole: -20db/dec magnitude loss and -90° phase shift. Capacitor → pole.
 - Zero: +20db/dec magnitude and +90° phase shift. Resistor → zero.

PLL Response vs. Damping


Phase Tracking vs. Damping

- Peaking at low and high damping factors → bad
- Damping ~ 1 → good compromise
- Phase Tracking → think “accumulated” jitter or phase error
- VCO frequency peaking (aka period jitter) similar to phase peaking

 PLL Transfer Function (Phase Out/In) vs. Damping



 
PLL Phase Transfer Function (FB/Ref) vs. Damping




Transient: Phase Error vs. Damping

- Less ringing and overshoot as $\zeta \rightarrow 1$
- Severe overdamping \rightarrow ringing and overshoot
- Ringing at high damping due to low oversampling (large R) – Gardner limit.

 Phase Response (T_{err}/T_{step}) to 8 nS Ref Phase Step



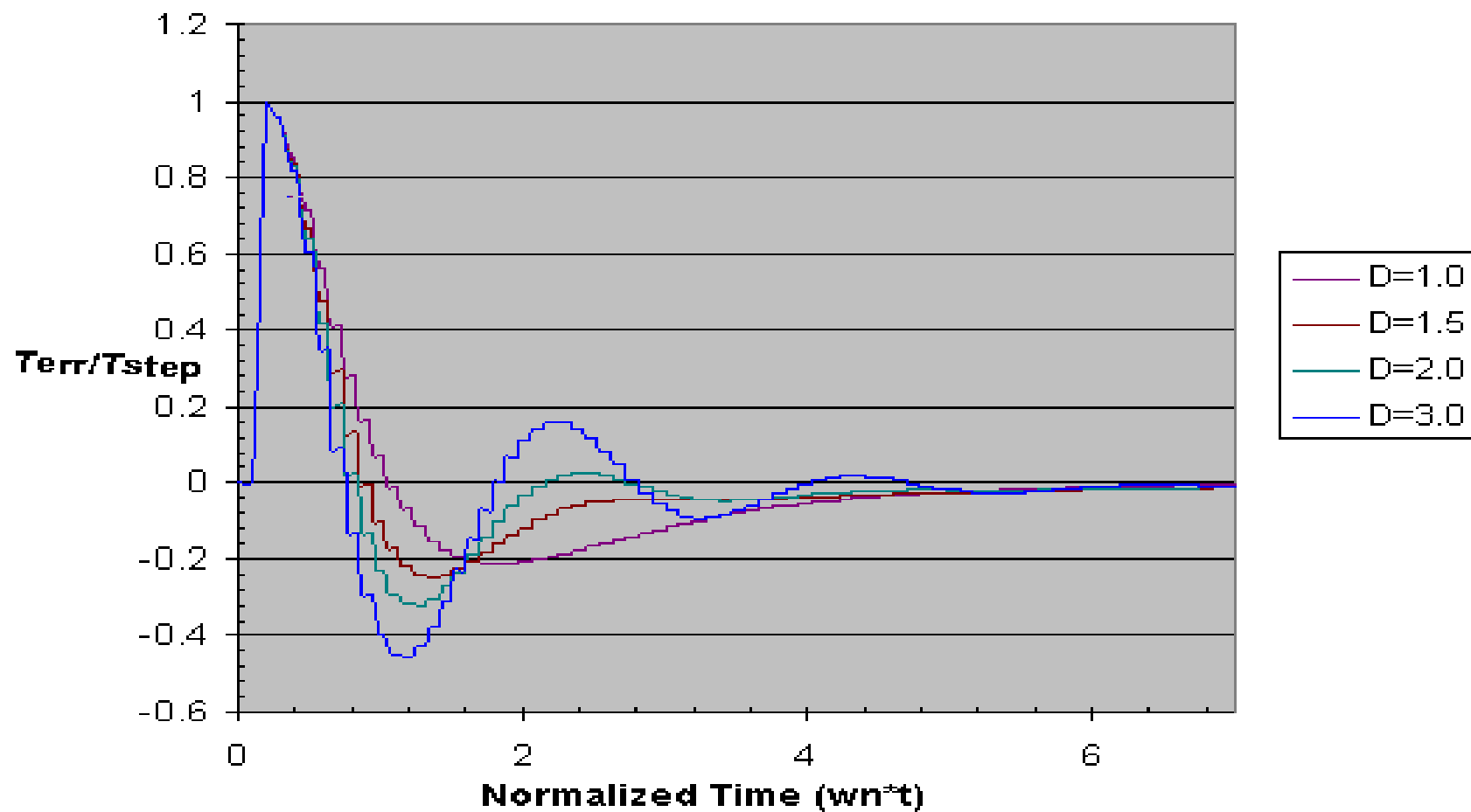
Phase Response (T_{err}/T_{step}) to 8 nS Ref Phase Step




VCO Jitter (df/f) vs. Damping

- Low damping \rightarrow less period jitter, slower response, more phase error
- High damping \rightarrow low oversampling (large R) causes oscillation

 VCO Freq (df/f) Response to 8 nS Ref Phase Step



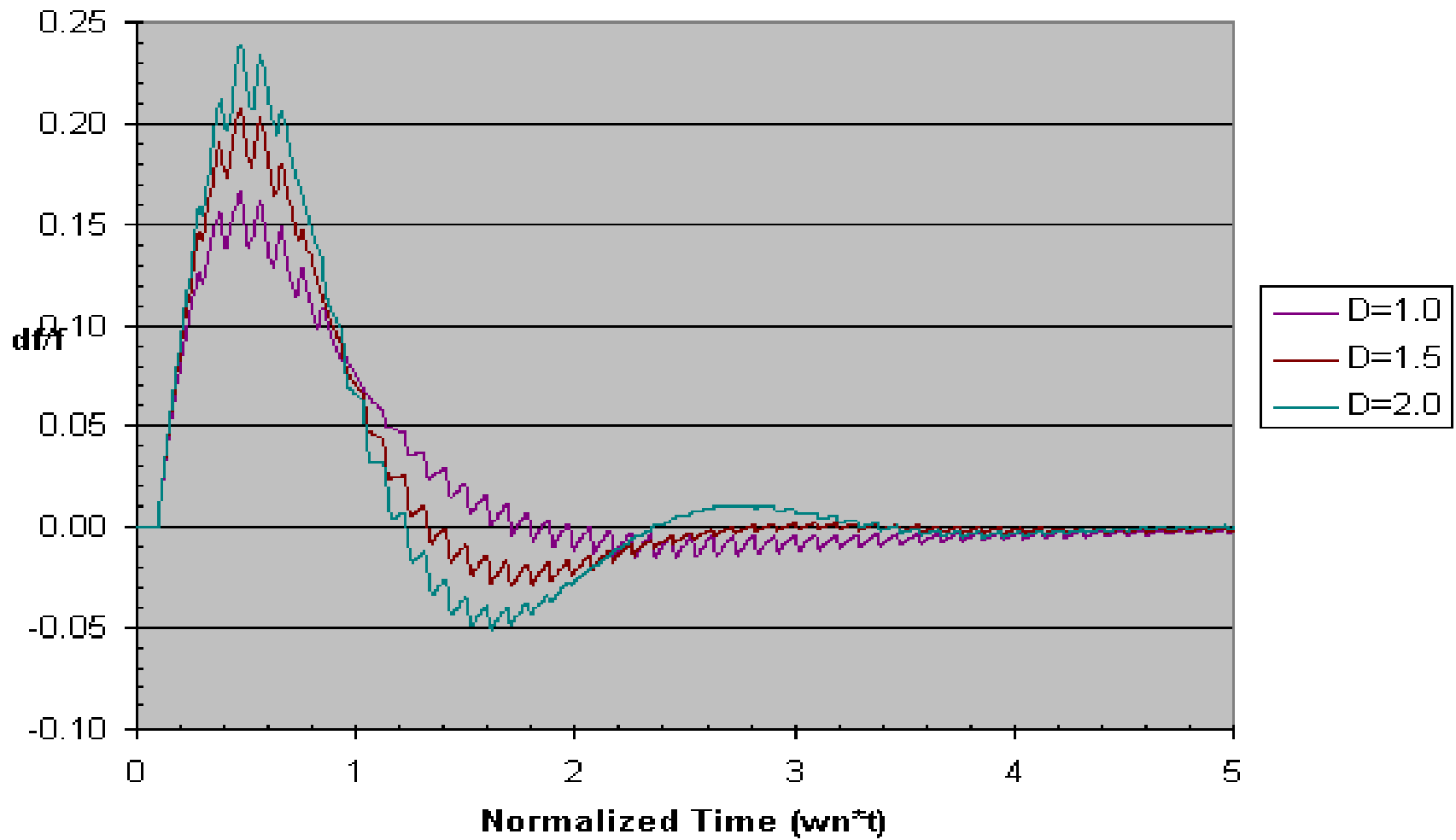VCO Freq (df/f) Response to 8 nS Ref Phase Step




PLL Response vs. Bandwidth

VCO Freq. Overshoot vs. Bandwidth

- Lower BW \rightarrow lower overshoot
- Higher OverSamplingRatio ($\omega_{\text{ref}}/\omega_n$) \rightarrow lower bandwidth(BW)
- Note: $\zeta \sim$ BW in these simulations

 Pct. Frequency Overshoot vs. Oversampling Ratio at Initial Lock



Phase Error (due to VCO Noise) vs. BW

- For random VCO noise (I.e. thermal): lower BW → higher accumulated phase error
- Why? More jittery VCO cycles before PLL starts to correct:

$$T_{\text{err}} \sim J_{\text{rms}} * \text{sqrt}(2\pi f_{\text{vco}}/\omega_n)$$


where

J_{rms} = std dev of VCO period jitter

- valid for damping ~ 1

- assume: $J_{\text{rms}} \sim 1/f_{\text{vco}} \rightarrow$ higher f , lower J_{rms}

 VCO Noise Tracking % (T_{err}/T_{ref}) vs. BW (ω_{VCO}/ω_n)




PLL Circuits

- Phase-Frequency Detector
- Charge-Pump
- Low-Pass Filter
- Voltage-Controlled Oscillator
- Level-Shifter
- Voltage Regulator

Phase-Frequency Detector(PFD)

PFD Block Diagram

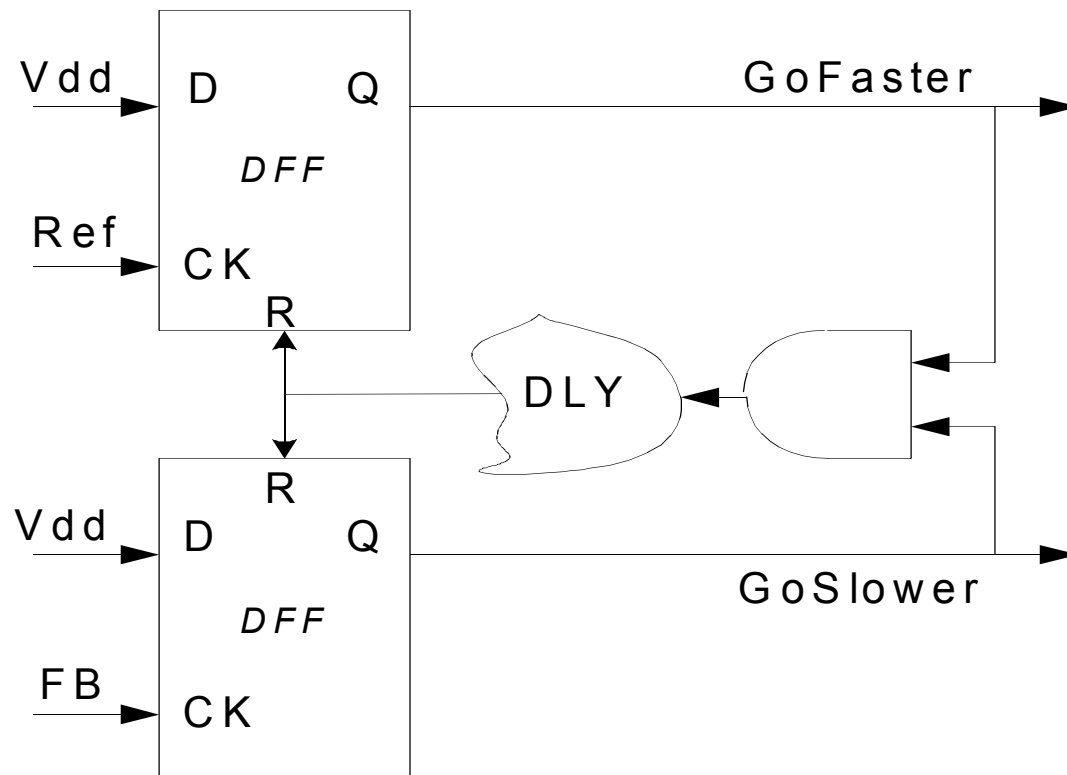- Edge-triggered - Input duty-cycle doesn't matter
- Pulse-widths proportional to phase error




PFD Logic States

- 3 and "1/2" Output states
- States:

GoFaster	GoSlower	Effect:
0	0	No Change
0	1	Slow Down
1	0	Speed Up
1	1	Avoid Dead-Zone

Example: PFD

 

Avoiding the Dead-Zone

- “Dead-zone” occurs when the loop doesn’t respond to small phase errors - e.g. 10 pS phase error at PFD inputs:
 - PFD cannot generate 10 pS wide *GoFaster* and *GoSlower* pulses
 - Charge-pump switches cannot turn on and off in 10 pS
 - Solution: delay reset to guarantee min. pulse width (typically > 150 pS)

Charge Pump(CP)


Charge Pump

- Converts PFD phase error (digital) to charge (analog)

- Charge is proportional to PFD pulse widths

$$Q_{cp} = I_{up} * t_{faster} - I_{dn} * t_{slower}$$

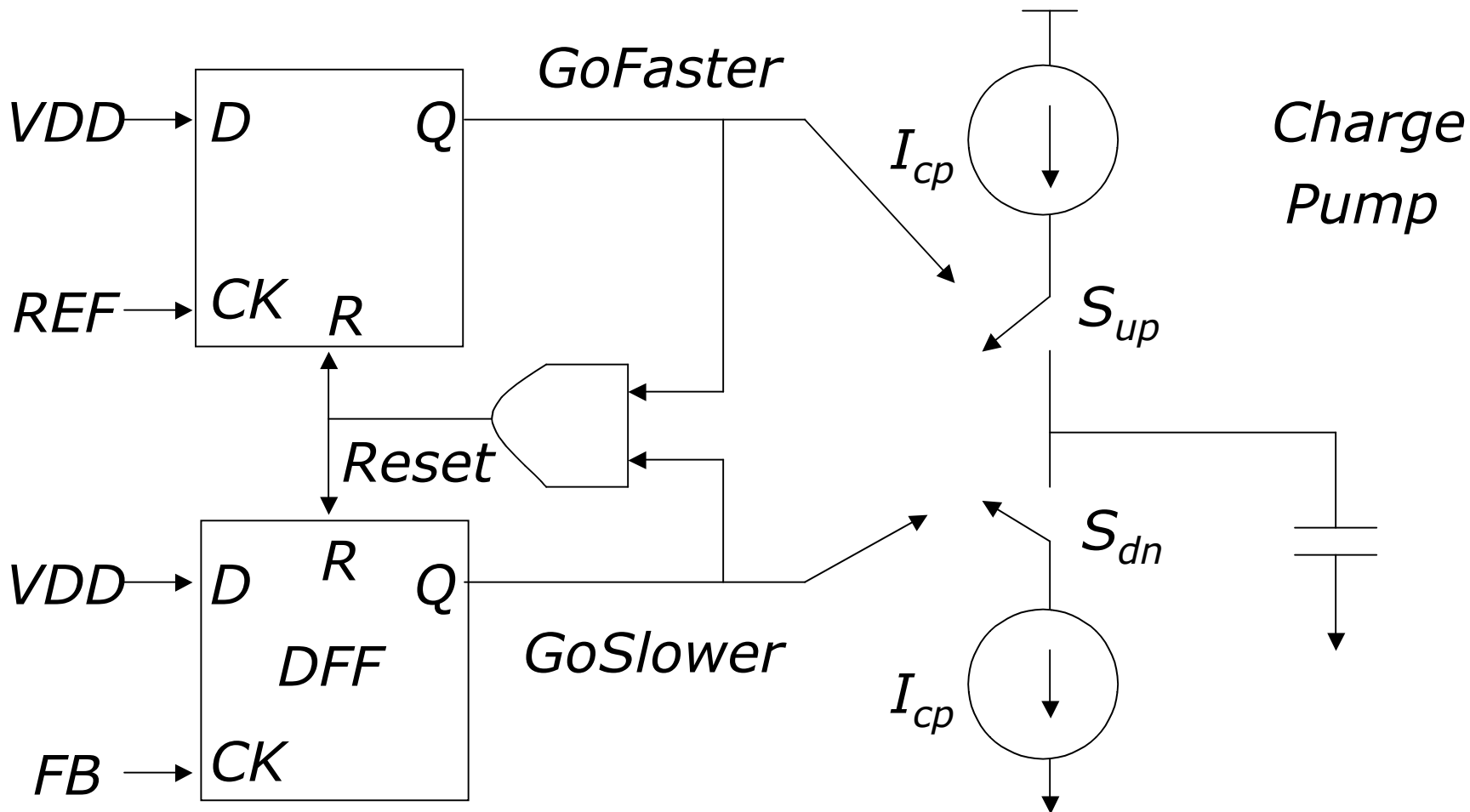- Q_{cp} is filtered/integrated in low-pass filter



Charge-Pump Wish List

- Equal *UP/DOWN* currents over entire control voltage range - reduce phase error.
- Minimal coupling to control voltage during switching - reduce jitter.
- Insensitive to power-supply noise and process variations – loop stability.
- Easy-to-design, PVT-insensitive reference current.
- Programmable currents to maintain loop dynamics (vs. M, f_{ref})?
- Typical: $1\mu\text{A}$ (mismatch) $< I_{\text{cp}} < 50\mu\text{A}$ (ΔV_{ctl})

Static Phase Error and CP Up/Down Mismatches

- Static Phase Error: in lock, net *UP* and *DOWN* currents must integrate to zero
 - If *UP* current is 2X larger, then *DOWN* current source must be on 2X as long to compensate
 - Feedback clock must lead reference for *DOWN* to be on longer
 - $T_{err} = T_{dn} - T_{up} = T_{reset} * (I_{up}/I_{dn} - 1)$

Static Phase Error and CP Up/Down Mismatches


- Phase error can be extremely large at low VCO frequencies (esp. if self-biased) due to mismatch in current mirrors (low $V_{gs} - V_t$)
- Increase V_{gs} or decrease ΔV_t (large $W \cdot L$)
- Typical static phase error < 100 pS

VCO Jitter and CP Up/Down Mismatches

- PFD-CP correct at rate of reference (e.g. 10nS).
- Most phase error correction occurs near reference rising edge and lasts < 200 pS, causing a control voltage ripple.
- This ripple affects the VCO cycles near the reference more than VCO cycles later in the ref cycle, causing VCO jitter.
- Typ. Jitter $\ll 1\%$ due to *Up/Down* Mismatches
- Avoid ripple by spreading correction over entire ref cycle. (Maneatis JSSC '03)


Simple Charge Pump

 - $R(\text{switches})$ varies with V_{ctl} due to body-effect
- Use CMOS pass-gate switches for less V_{ctl} sensitivity
- Long-channel current sources for matching and higher R_{out}




Charge Pump: const I with amp

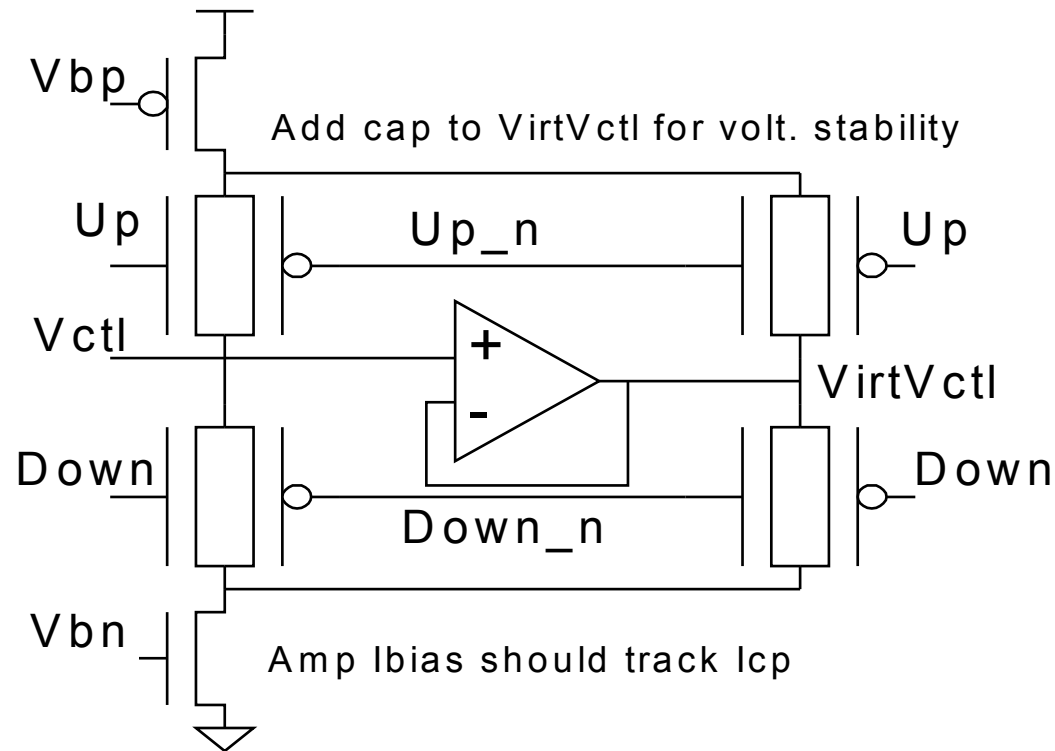- Amp keeps V_{ds} of current sources constant (Young '92)
- Amp sinks "waste" current when UP, DOWN off




Charge Pump – switches reversed

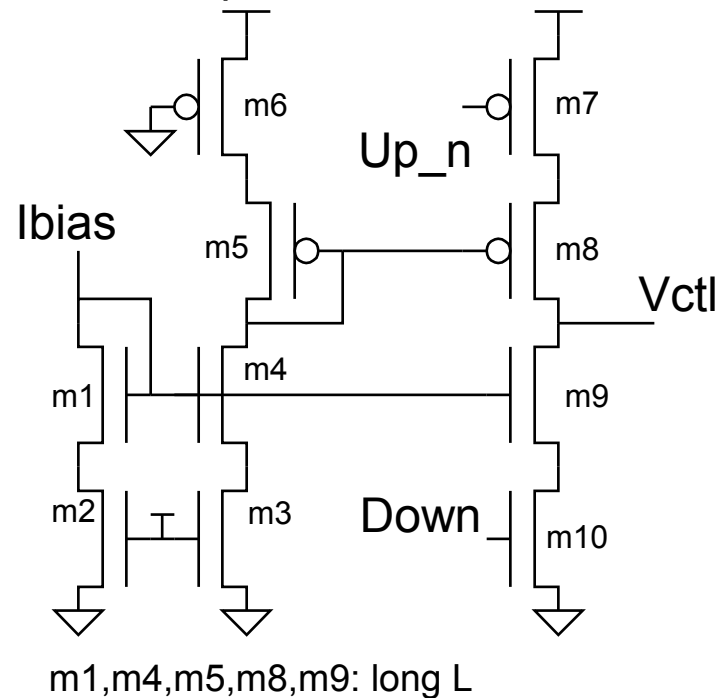- Switches closer to power rails reduce noise and V_{ctl} dependence $\rightarrow I_{cp}$ not constant with up/down



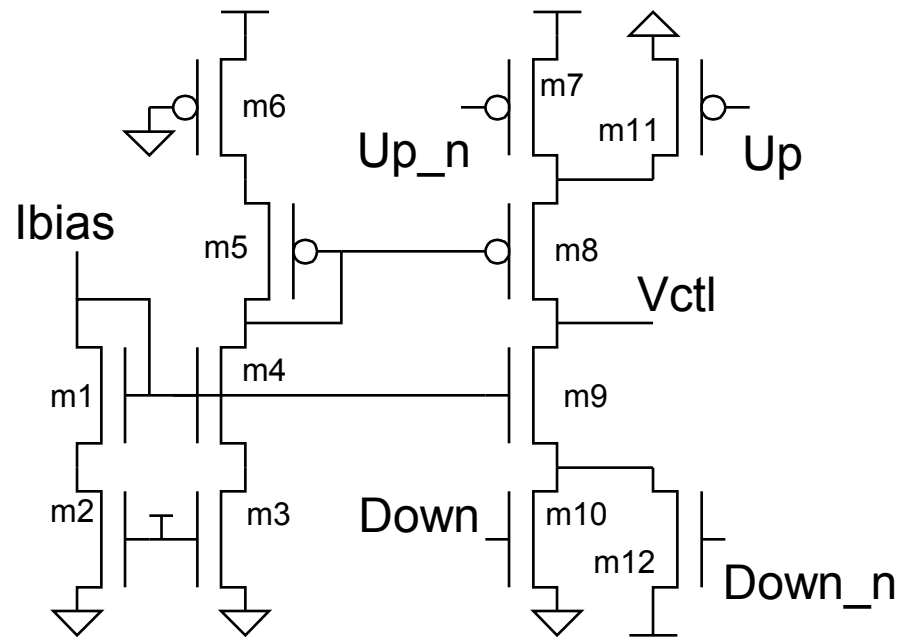
Charge Pump: switches reversed with fast turn-off (Ingino '01)



m1,m4,m5,m8,m9: long L
m11, m12: faster turn-off


Simple Charge-Pump Bias

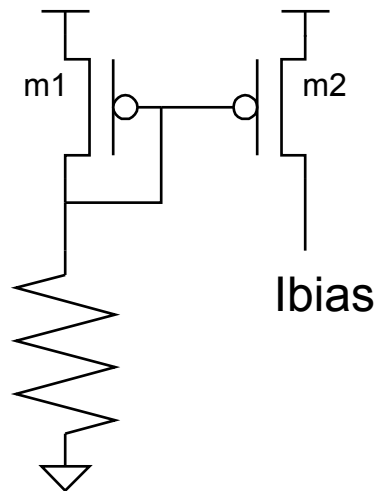- $I_b \sim (V_{dd} - V_t)/R$
- I_b dependent on PVT
- Prefer low- V_t , moderate-to-long L for process insensitivity, large W/L for low gate-overdrive
- Pro: Simple, stable. Con: V_{dd} dependence




VDD-independent I_bias

 - $I_b \sim 1/R^2$
- Con: requires start-up circuit not shown



Bandgap-based Ibias

 
- $I_b \sim V_{ref}/R$
- Con: feedback loop may oscillate
 - cap added to improve stability
- Pro: VDD-independent, mostly Temp independent



Low-Pass Filter (LPF)


Low-Pass Filter

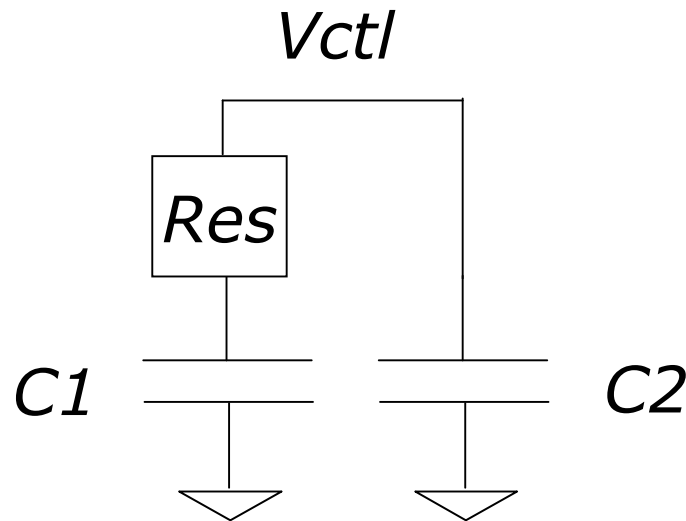- Integrates charge-pump current onto C_1 cap to set average VCO frequency (“integral” path).
- Resistor provides instantaneous phase correction w/o affecting avg. freq. (“proportional” path).
- C_2 cap smoothes large IR ripple on V_{ctl}
- Typical value: $0.5k < R_{lpf} < 20k\Omega$



Feed-Forward Zero: eliminate R

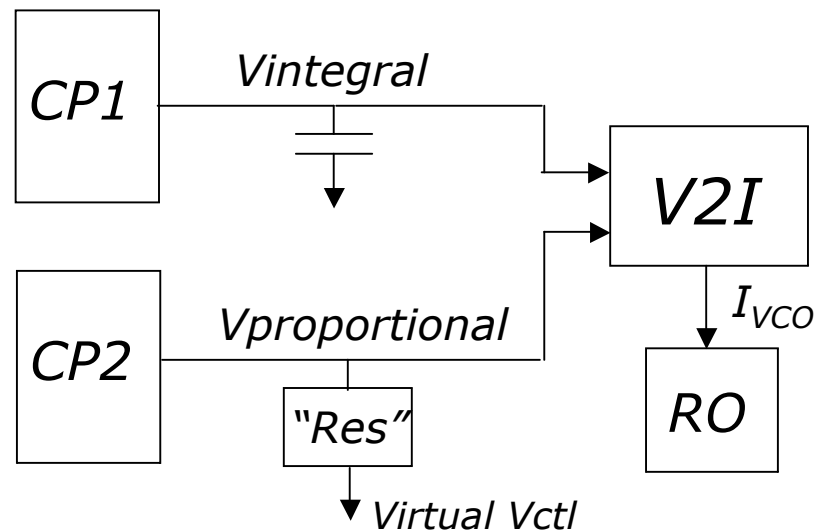
- Resistor provides an instantaneous IR on the control voltage causing the VCO V2I to generate a current bump on the oscillator input
- Eliminate R → Add parallel CP path into V2I
- See Maneatis JSSC '96 or '03 for example



Low-Pass Filter Smoothing Cap(C_2)

- “Smoothing” capacitor on control voltage filters CP ripple, but may make loop unstable
- Creates parasitic pole: $\omega_p = 1/(R C_2)$
- $C_2 < 1/10 * C_1$ for stability
- $C_2 > 1/50 * C_1$ for low jitter
- Smoothing cap reduces “IR”-induced VCO jitter to $< 0.5\%$ from 5-10%
- $\Delta f_{vco} = K_{vco} I_{cp} T_{err} / C_2$
- Larger C_2/C_1 increases phase error slightly

Pct. Frequency Overshoot vs. LPF C2/C1

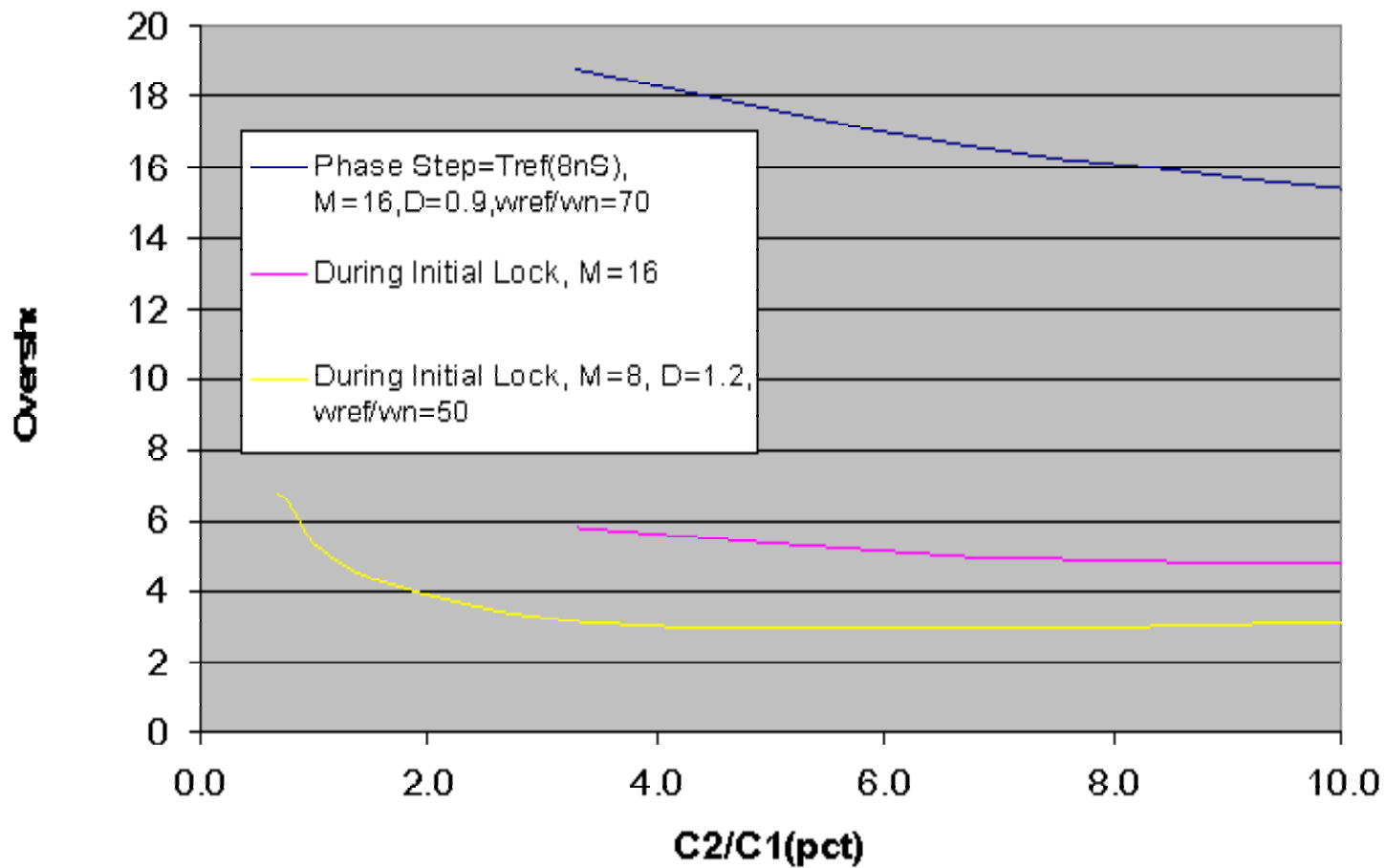

Low-Pass Filter Capacitors

- At $\leq 130\text{nm}$, thin-gate oxide leakage is huge:
 - $I_{\text{leak}} \sim V_{\text{gate}}^{4.5}$
 - NMOS leakier than PMOS
 - Weak temperature dependence
 - I_{leak} vs. $t_{\text{ox}} \rightarrow \sim 2\text{-}3\text{X}$ per Angstrom
- Use metal caps or thick-gate oxide caps to reduce leakage
- Metal caps use 10X more area than thin gate caps
 - Use minimum width/spacing parallel lines
 - Hard to LVS - Check extracted layout for correct connectivity

Low-Pass Filter Capacitors

- Even thick gate oxide may still leak too much
- Large filter cap (C_1) typically ranges from 50pF to 400 pF
- C_1 cap BW may be low as $\sim 10X$ PLL BW for nearly ideal behavior
- Min C_2 BW set by T_{ref}
- Cap BW $\sim 1/RC \sim 1/L^2$
- Gate cap not constant with V_{gs}

Voltage-Controlled Oscillator (VCO)

Voltage-Controlled Oscillator

- VCO usually consists of two parts: control voltage-to-control current ($V2I$) circuit and current-controlled ring oscillator (ICO)
- VCO may be single-ended or differential
- Differential design allows for even number of oscillator stages if differential-pair amps used for delay cells
- $V2V$ may be used instead to generate bias voltages for diff-pair amps

PLL Suppression of VCO Noise

- PLL acts like a high-pass filter in allowing VCO noise to reach PLL output
- Need noise-immune VCO to minimize jitter
 - Feedback loop cannot react quickly.
- Power-supply noise is largest source of VCO noise

VCO Design Concerns


- Min low-frequency power-supply sensitivity
 $< 0.05\%$ per %dVDD \rightarrow reduce phase error
- Min high-frequency power-supply sensitivity
 $< 0.1\%$ per %dVDD \rightarrow reduce period jitter
 Note: this is 10X better than normal INV
- Low substrate-noise sensitivity \rightarrow reduce ΔV_t
 - unnecessary in SOI
- Thermal noise (kT)
 - typically $< 1\%$ VCO period at high frequency

VCO Design Concerns

- Large frequency range to cover PVT variation:
 - 3-5X typical
- Single-ended or differential?
 - use differential for 50% duty-cycle
- Vco gain ($f_{vco} = K_{vco} * V_{ctl}$) affects loop stability
- Typical VCO gain: $K_{vco} \sim 1-3X * f_{max}$
- More delay stages → easier to initiate oscillation
 - Gain(DC) > 2 for 3 stages
 - Gain(DC) > sqrt(2) for 4 stages

VCO w/“pseudo-differential” current-starved inverters

- Need odd # of stages
- Feedback INV \rightarrow usually weaker by $\sim 4X$
- “Vdd” for inverters is regulated output of V2I

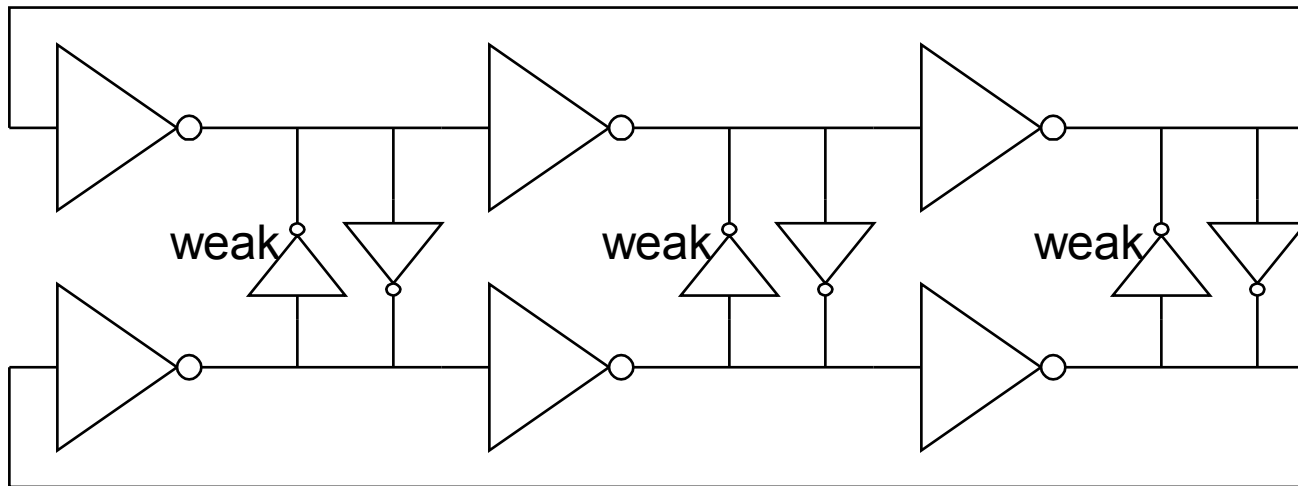


VCO V-to-I Circuits

- Converts V_{ctl} to I_{ctl}
- May generate additional V_{bias} for oscillator
- May use internal feedback to set VCO swing
- Provides power-supply rejection \rightarrow fets in deep saturation or amp-based internal feedback
- Filters high-frequency V_{ctl} ripple w/another cap
- Adds parasitic pole \rightarrow $\text{BW}(\text{V2I}) \gg \text{BW}(\text{PLL})$
- Digital *Range* settings allow for control of VCO gain and V_{ctl} range \rightarrow must overlap ranges


Simple V2I

 - Minimal filtering of V_{ctl} ripple
- Keep long-channel current source in saturation
- Cap adds parasitic pole $\rightarrow \omega_p = 1/(R_{vco} * C)$
- Typical Cap Size: $0.5 \text{ pF} < C < 5 \text{ pF}$
- Reference V_{ctl} to same potential as LPF caps



V2I w/Feedback (V. von Kaenel (JSCC '96))

 
- Feedback \rightarrow amp provides good low-freq power-supply rejection
- Cap to Vdd provides good high-freq rejection
- Start-up needed
- Stability concern?



Differential VCO's


VCO: simple differential delay

 - DC gain $\sim g_{m1} * R$
- Hard to get enough gain w/o large resistor
- Tail current controls delay – V2I needed?




VCO: differential delay w/symmetric load (Maneatis '96)

 - Loads acts like resistor over entire voltage swing
- Widely used but requires two bias voltages



V2I: replica bias - symmetric load

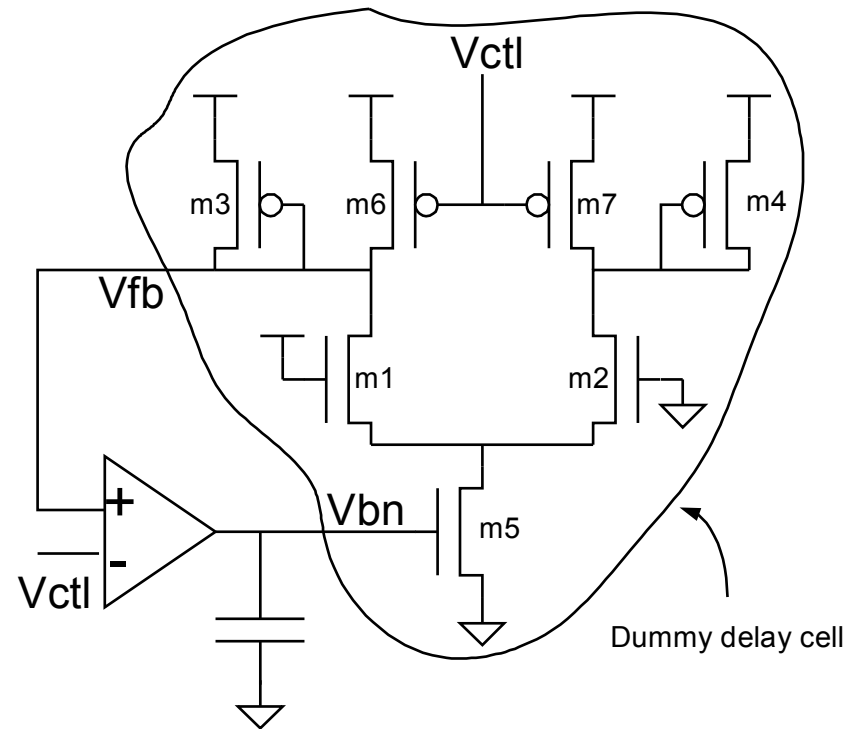- $V_{\text{swing}} = V_{\text{ctl}}$ (Maneatis '96)
- Amp provides DC power-supply rejection
- Stable, but getting high BW and good PSRR tricky




VCO Level-Shifter

- Amplify limited-swing VCO signals to full-rail
 - typically from 0.4-0.7V to VDD
- Maintain 50% duty-cycle
 - usually +/- 3%
 - difficult to do over PVT and frequency
- Insensitive to power-supply noise
 - < 0.5 % per % dVDD
- Which power-supply? Analog or digital?
 - usually digital

VCO: Level-Shifter

 - Need sufficient gain at low VCO frequency
- Use NMOS input pair if VCO swing referenced to VSS for better power-supply rejection
- Net "zn" should swing almost full-rail to switch output inverter



Feedback Divider

Feedback Divider (FBDIV)

- Divide VCO by $N \rightarrow f_{\text{ref}} = f_{\text{vco}}/N$
- Divider may be internal to PLL or after CPU clock tree
- Max FBDIV frequency should be greater than max VCO frequency to avoid “run-away”
- Minimize FBDIV latency to reduce VDD-induced jitter seen at phase detector
- Loop Phase Margin Degradation $\sim \omega_n T_{\text{dly}}$
 - usually insignificant


Feedback Divider

- Two common types of dividers:
 - Asynchronous cascade of div-by-2's
 - Synchronous counter – typically used

Asynchronous Divide-by-2

- Pro: fast, simple
- Pro: small area
- Con: long latency for large divisors
- Con: divide by powers of 2 only
- Can be used as front-end to synchronous counter divider to reduce speed requirements

Feedback Divider: cascade of div-by-2's

 

Counter-Based Divider

- Pro: divide by any integer N
- Pro: constant latency vs. N
- Pro: low latency
- Pro: small area \rightarrow Binary-encoded.
- Con: slow if using ripple counter \rightarrow don't
- Con: output may glitch \rightarrow delay (re-sample) output by one cycle to clean up glitch

VDDA Voltage Regulator

Voltage Regulator/Filter


- Used to filter power-supply noise
 - typically > 20 dB (10x) PSRR over entire frequency range
 - desire 30+ dB
- Secondary purpose is to set precise voltage level for PLL power supply
 - usually set by bandgap reference

Voltage Regulator


- Bandgap reference generates a voltage reference ($\sim 1.2V$) that is independent of PVT
 - relies on parasitic diodes (vertical PNP)
- Regulator output stage may be source-follower (NFET) or common-source amp (PFET)
 - source-follower requires more headroom (and area?) but is more stable
 - common-source amp may be unstable without Miller capacitor or other compensation
- Beware of large, fast current spikes in PLL load (i.e. when changing PLL frequency range)

Bandgap Reference w/Miller Cap

 - Stability and PSRR may be poor w/o Miller cap
- Miller cap splits poles. Can also add R in series w/Cc for more stability (Razavi '00)



Voltage Regulator for VDDA

 

Advanced Concepts: Self-Biased PLL

- Conventional PLL: loop dynamics depends on I_{cp} , R_{lpf} , C_{lpf} , K_{vco} and $FBDiv$. These do not necessarily track.
- Why not generate all bias currents from the $I(vco)$ and use a feed-forward zero to eliminate the resistor. Everything tracks. (Maneatis JSCC '03)
- Con: start-up, stability
- Pro: reduces PVT sensitivity

Example Circuit Parameters

- $V_{DD}=1.2V$, $f(\text{max})-f(\text{min}) = 3 \text{ GHz}$
- $K_{vco} = 5\text{GHz}/V \rightarrow$ usable V_{ctl} range (0.6V)
- $I_{cp} = 20 \text{ uA}$
- $R_{l_{pf}}=2500 \text{ Ohm}$
- $C_1=75 \text{ pF} \rightarrow$ Area(metal) $\sim 275\text{um} \times 275\text{um}$
- $C_2=5 \text{ pF}$
- $0.85 < \zeta < 1.2$
- $1.5 \text{ MHz} < \omega_n/2\pi < 2.1 \text{ MHz}$
- $T_{acq} \sim 5 \text{ uS} \rightarrow T_{aqc} = \sim 2CdV/I$

Real-world PLL Failures

PLL Problem

- Problem: 3-stage PMOS diff-pair VCO wouldn't oscillate at low frequencies. When VCO finally started up at high V_{ctl} , it outran FBDIV.
- Cause: leaky, mis-manufactured loads in delay cell reduced gain of delay element < 2
- Solutions:
 - increase L of load devices for higher gain
 - add more VCO stages to reduce gain requirements

PLL Problem

- Problem: VCO stuck at max frequency at power-on.
- Cause: PLL tried to lock before VDD was stable. Because VCO couldn't run fast enough to lock at low VDD, V_{ctl} saturated. When VDD finally stabilized, $V_{ctl} = VDD$, causing a maxed-out VCO to outrun FBDIV.
- Solution: maintain PLL RESET high until VDD is stable to keep V_{ctl} at 0V.

PLL Problem

- Problem: VCO stuck at max frequency after changing power-modes.
- Cause: Feedback DIV could not run fast enough to handle VCO overshoot when locking to a new frequency or facing a reference phase step.
- Solutions:
 - limit size of frequency steps
 - increase speed of Feedback DIV

PLL Problem

- Problem: PLL would not lock.
- Cause: Feedback DIV generated glitches causing PFD to get confused.
- Solution: add re-sampling flop to output of feedback DIV to remove glitches.

PLL Problem

- Problem: PLL output clock occasionally skipped edges at low VCO frequencies
- Cause: VCO level-shifter had insufficient gain when VCO swing was close to V_t .
- Solutions:
 - increase W of diff-pair inputs
 - use low- V_t devices

PLL Problem

- Problem: VCO jitter was huge at some divider settings and fine at others.
- Cause: Integration team connected programmable current sources backward.
- Solution: write accurate verilog model that complains when inputs are out-of-range.

PLL Problem

- Problem: PLL jitter was poor at low freq and good at high freq.
- Cause: V_{ctl} was too close to V_t at low frequency.
- Solution: Run VCO at 2X and divide it down to generate slow clocks.

PLL Problem

- Problem: RAMDAC PLL had large accumulated phase error which showed up as jitter on CRT screen.
- Cause: PLL bandwidth was too low, allowing random VCO jitter to accumulate.
- Solution: increase bandwidth so that loop corrects before VCO jitter accumulates.

PLL Problem

- Problem: PLL had poor peak-peak jitter, but good RMS jitter.
- Cause: digital VDD pin in package adjacent to PLL's analog VDD coupled digital VDD noise to analog VDD during certain test patterns.
- Solution: Remove wirebond for adjacent digital VDD pin.

PLL Problem

- Problem: large static offset.
- Cause: designer did not account for gate leakage in LPF caps.
- Solutions:
 - switch to thick-gate oxide caps
 - switch to metal caps

PLL Problem

- Problem: VCO period jitter = +/- 20%, modulated at a fixed frequency.
- Cause: Unstable V2I internal feedback loop caused by incorrect processing of stabilizing caps.
- Solutions:
 - correct manufacturing of capacitors
 - add more caps

PLL Problem

- Problem: bandgap reference was stable in one process but oscillated in a different process with similar feature sizes.
- Cause: compensation caps for 2-pole feedback system with self-bias were too small.
- Solution: make compensation caps 3X larger.

Uncle D's PLL Top 5 List

- 5. Maintain damping factor ~ 1
- 4. VDD-induced VCO noise – loop can't do the work for you
- 3. Leaky gate caps will cost you your job
- 2. Make FB DIV run faster than VCO
- 1. Observe VCO, FBCLK, REF, clkTree on differential I/O pins – you can't fix what you can't see!

Appendices

Appendices

- Appendix A: Design for Test
- Appendix B: Writing a PLL spec
- Appendix C: Additional PLL material
- Appendix D: Paper References
- Appendix E: Monograph References

Design for Test

Design for Test Overview

- Measuring Jitter
- Analog Observation
- Probing

Measuring Jitter: Power-Supply Noise Sensitivity

- Induce noise on-chip with VDD-VSS short
 - need off-chip frequency source or on-chip FSM to control noise generator
 - How to measure induced noise magnitude?
- Induce noise on board
 - capacitively couple to VDDA
 - hard to get it past filtering and attenuation
 - how much makes it to PLL?
 - VDDA inductance? – wire-bond, flip-chip

Routing: From PLL to Board

- Differential IO outputs highly desirable
- Types of IO – use highest-speed available
- Divide VCO to reduce board attenuation only if necessary → make divider programmable
- Measuring duty-cycle
 - Divide-by-odd-integer
 - Mux to select either true or inverted clock
- Minimize delay on-chip from PLL to IO
- Ability to disable neighboring IO when measuring jitter
- Avoid coupling in package and board

General Test Hardware

- High-bandwidth scope:
 - 4-6 GHz real-time
 - \$50-60k
 - e.g. Agilent, Tektronix, LeCroy
- Differential high-speed probes:
 - 3-6 GHz BW
 - \$3-6k
- Active pico-probes and passive (DC) probes for micro-probing PLL
- Avoid large GND loops on probes

Jitter Hardware/Software

- Jitter Analysis tools:
 - e.g. Wavecrest, Tek(Jit2), Amherst Design
- Jitter measurement types:
 - Period jitter histogram
 - Long-term jitter
 - Cycle-to-adjacent cycle jitter
 - Half-period jitter
 - Jitter FFT - limited by Nyquist – aliasing
- Scope memory depth

Miscellaneous Jitter Measurements

- Open-loop vs. Closed-loop Jitter
 - disable loop-filter → does PLL jitter change?
- Mux *Ref* into PLL observation path for jitter calibration
 - Is *Ref* jitter worse after coming from PLL compared to before it enters the chip?
- Observe “end-of-clock tree” for jitter and duty-cycle distortion
- Observe *Fbclk* for jitter and missing edges

Measuring PLL Loop Dynamics

- Modulate reference frequency, measuring long-term PLL jitter. Sweep modulation frequency to determine bandwidth and damping.
 - e.g. Wavecrest
- Spectrum analyzer
 - look for noise suppression in frequency range close to signal peak
 - difficult if noisy setup

Measuring Phase Error

- Hard to do!
- *Fbclk* available for observation?
- Need to acct. for *Fbclk* delay from PLL to IO – depends on PVT.
- Solutions:
 - route *Fbclk* off-chip to pkg and match input delay with *Ref. Fbclk/Ref* skew at pins \sim T_{err} at PFD.
 - measure T_{err} on-chip – send out narrow pulses – narrow pulses disappear.
 - measure T_{err} on-chip with A/D. Complex.
 - mux *Fbclk* and ref into same path. Compare both to external reference.

Analog Observation

- Analog observation IO pins for debug and characterization
 - may force internal analog nets as well if bi-directional pin
 - low-bandwidth requirements → low MHz or kHz
 - isolate analog nets with unity-gain buffer or resistor and pass-gates w/solid pull-down
 - drive analog pins to known value when not in use
 - tri-state analog pin for ESD leakage testing
 - ESD protection (CDM and HBM) may cause IO leakage

Probing On-chip

- If not flip-chip, then put probe pads on top-layer metal.
- Probe pad size $>1\mu\text{m} \times 1\mu\text{m}$. Prefer $> 2\mu\text{m} \times 2\mu\text{m}$.
- Place probe pad on a side-branch of the analog signal to avoid breaking wire with probe.
- Separate probe pads to allow room for multiple probes.
- FIB: can add probe pad, add or remove wires.
 - need room and luck
- FIB: can FIB SOI flip-chip from back of wafer if enough room around lower-level wires.

Writing a PLL Spec

Spec Overview

- Area, physical integration
- Technology issues
- Power-supply voltage
- Performance metrics
- Logic interface

Physical Integration

- Area, aspect ratio?
- What metal layers are available?
- Digital signal routing allowed over PLL?
- Where is PLL located on chip?
- Wire-bond or flip-chip?

Semiconductor Process

- 90nm, 130nm, 180nm?
- Bulk vs. SOI? SOI body-ties?
- Nwell vs. twin-well?
- Epi substrate?
- Accumulation-mode capacitors?
- Gate-oxide thickness? Capacitance density and leakage.
- Dual-gate oxide available? Leakage.
- Poly density requirements?
- Low- V_t available?
- Resistor types? Poly? Diffusion?

Power-Supply

- Separate analog VDDA? What voltage? 1.8V? 2.5V? Higher than core voltage?
- Separate analog VSSA?
- Wire-bond or flip-chip? Package Type?
- What type of VDDA filtering on board? Ferrite bead? What cap sizes?
- Min, max VDDA? DC variation? AC variation? Natural frequency ($1/LC$) of VDDA?

Performance

- Reference clock frequency? Range?
- Min/Max VCO Frequency?
- Duty cycle?
- Period Jitter?
- Fixed jitter spec or pct of period?
- Cycle-to-adjacent cycle jitter spec?
- Half-cycle jitter spec?

Performance

- Max Frequency overshoot while settling?
- Static phase error?
- Dynamic phase error?
- Loop bandwidth?
- Time to acquire initial lock?
- Time to re-acquire lock after frequency change?
- Power Dissipation?

Logic Interface

- *Reset* available?
- *PowerOK* available?
- VCO/CP/R range settings allowed?
- Clock glitching allowed when switching VCO frequency ranges?
- Level-shift and buffer PLL inputs/outputs?
- Different power domains?

Example Design Specs

- $f(ref) = 125 \text{ MHz}$
- $8 < FBDiv < 16 \rightarrow 1 \text{ GHz} < f(vco) < 2 \text{ GHz}$
- $\zeta > 0.7$ – not constant w/ $FBDiv$
- $1 \text{ MHz} < \omega_n/2\pi < f(ref) / 20$
- Pk-Pk Jitter $< +/- 2.5\%$ w/ $dVdd = 50\text{mV}$
- $T_{lock} < 10 \text{ uS}$
- FreqOvershoot $< 15\%$ w/1-ref-cycle phase step
- Static Phase Error $< +/- 200 \text{ pS} \rightarrow Icp \text{ mismatch} < 50\%?$

References

Paper References

- [1] B. Razavi, *Monolithic Phase-Locked Loops and Clock-Recovery Circuits*, IEEE Press, 1996. – collection of IEEE PLL papers.
- [2] I. Young *et al.*, “A PLL clock generator with 5 to 110 MHz of lock range for microprocessors,” *IEEE J. Solid-State Circuits*, vol. 27, no. 11, pp. 1599-1607, Nov. 1992.
- [3] J. Maneatis, “Low-Jitter Process-Independent DLL and PLL Based on Self-Biased Techniques”, *IEEE J. Solid-State Circuits*, vol. 31, no. 11, pp. 1723-1732. Nov. 1996.
- [4] J. Maneatis, “Self-Biased, High-Bandwidth, Low-Jitter 1-to-4096 Multiplier Clock Generator PLL”, *IEEE J. Solid-State Circuits*, vol. 38, no.11, pp. 1795-1803. Nov. 2003.
- [5] F. Gardner, “Charge-pump phase-lock loops,” *IEEE Trans. Commun.*, vol COM-28, no. 11, pp 1849-1858, Nov. 1980.
- [6] V. von Kaenel, “A 32- MHz, 1.5mW @ 1.35 V CMOS PLL for Microprocessor Clock Generation”, *IEEE J. Solid-State Circuits*, vol. 31, no. 11, pp. 1715-1722. Nov. 1996.

Paper References (cont.)

- [7] I. Young, "A 0.35um CMOS 3-880MHz PLL N/2 Clock Multiplier and Distribution Network with Low Jitter for Microprocessors", ISSCC 1997 Digest of Tech. Papers, session 20.1, pp. 330-331.
- [8] J. Ingino *et al*, "A 4-GHz Clock System for a High-Performance System-on-a-Chip Design", IEEE J. Solid-State Circuits, vol. 36, no. 11, pp. 1693-1698. Nov. 2001.
- [9] A. Maxim, *et al.*, "A Low-Jitter 125-1250 MHz Process-Independent CMOS PLL Based on a Sample-Reset Loop Filter", 2001 ISSCC Digest Of Tech. Papers, pp. 394-395.
- [10] N.Kurd, *et al.*, "A Replica-Biased 50% Duty Cycle PLL Architecture with 1X VCO", 2003 ISSCC Digest of Tech. Papers, session 24.3, pp.426-427.
- [11] K. Wong, *et al.*, "Cascaded PLL Design for a 90nm CMOS High Performance Microprocessor", 2003 ISSCC Digest of Tech. Papers, session 24.3, pp.422-423.
- [12] M. Mansuri, *et al.*, "A Low-Power Adaptive-Bandwidth PLL and Clock Buffer With Supply-Noise Compensation", IEEE J. Solid-State Circuits, vol. 38, no.11, pp. 1804-1812. Nov. 2003.

Paper References (cont.)

- [7] A. Maxim, "A 160-2550 MHz CMOS Active Clock Deskewing PLL Using Analog Phase Interpolation", ISSCC 2004 Digest of Tech. Papers, session 19.3, pp. 346-347.
- [8] Jerry Lin *et al*, "A PVT Tolerant 0.18MHz to 660MHz Self-Calibrated Digital PLL in 90nm CMOS Process", ISSCC 2004 Digest of Tech. Papers, session 26.10, pp. 488-489.

Monograph References

- [1] B. Razavi, *Design of Analog CMOS Integrated Circuits*, McGraw-Hill, 2001.
- [2] R. Best, *Phase-Locked Loops*, McGraw-Hill, 1993.
- [3] R. Dorf, *Modern Control Theory*, 4th Edition, Addison-Wesley, 1986.
- [4] P. Gray & R. Meyer, *Analysis and Design of Analog Integrated Circuits*, 3rd Edition, J. Wiley & Sons, 1993.
- [5] K. Bernstein & N. Rohner, *SOI Circuit Design Concepts*, Kluwer Academic Publishers, 2000.
- [6] A. Hajimiri & T. Lee, *The Design of Low Noise Oscillators*, Kluwer Academic Publishers, 1999
- [7] T. Lee, *The Design of CMOS Radio-Frequency Integrated Circuits*, Cambridge University Press, 1998.
- [8] F. Gardner, *Phaselock Techniques*, 2nd Edition, New York, Wiley & Sons, 1979